



THE TECHNICAL UNIVERISTY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF COMPUTER SCIENCE & INFORMATION TECHNOLOGY
DIPLOMA IN INFORMATION COMMUNICATION TECHNOLOGY
(DICT 12M FT/EV)

EEE 2140: ELECTRONICS

END OF SEMESTER EXAMINATION

SERIES: APRIL 2013

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

This paper consists of **FIVE** questions. Attempt question **ONE** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **TWO** printed pages

Question One (Compulsory)

- a) Derive from the first principles the equation of the output voltage of a differentiator and integrator using OP – AMP. **(8 marks)**
- b) With the aid of symbolic diagrams, briefly explain the operations of the following Thyristors SCR, DIAC and TRIAC **(12 marks)**

Question Two

- a) With the aid of circuit diagrams, derive the gains of inverting and non-inverting amplifiers using operational amplifiers. **(10 marks)**
- b) Calculate the output voltage of a summing amplifier for the following sets of input voltages and

resistors. ($R_f = 0.1M\ \Omega$ in all cases)

(i) $V_1 = +1V, V_2 = +2V, V_3 = 3V$

$R_1 = 50K\ \Omega, R_2 = 01M\ \Omega, R_3 = 0.1M\ \Omega$

(ii) $V_1 = -2V, V_2 = +3V, V_3 = +3V$

$R_1 = 20K\ \Omega, R_2 = 50K\ \Omega, R_3 = 0.1M\ \Omega$

(10 marks)

Question Three

- a) A comparator circuit is fabricated using an OP – AMP. $V_{CC} = 9V, R_1 = 200K\ \Omega, R_2 = 100K\ \Omega + V_{SAT} = +12V$ and $-V_{SAT} = -12V$.
- (i) If $V_{IN} = 3V$ determine the output voltage of the comparator.
- (ii) If $V_{IN} = 4V$ determine the output voltage of the comparator
- (iii) If the resistor are interchanged and $V_{IN} = 4V$, determine the nature of the output voltage. **(10 marks)**
- b) With the aid of a circuit diagram, explain the operation of a class A, Temperature stabilized transistor amplifier **(10 marks)**

Question Four

- a) Using a graph show all the operational parameter of an SCR and explain each of them. **(10 marks)**
- b) State at least **FIVE** applications of Zener diodes. **(5 marks)**
- c) With the aid of circuit diagram briefly explain the operation of a Zener diode regulator. **(5 marks)**

Question Five

- a) An inverting amplifier using OP-AMP has an input $v_i = -0.2 \sin \omega t$. If the amplifier offer a gain of -100 .
- (i) Determine the expression for the output of the amplifier
- (ii) Draw the sketch of the output signal
- (iii) Determine the values of R_{in} and R_f which will give the amplifier the gain. **(10 marks)**

b) Explain at least **FIVE** ideal properties of an Operational Amplifier.

(10 marks)