



THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

(A Constituent College of Jkuat)

*Faculty of Engineering and Technology in Conjunction with Kenya
Institute of Highways and Building & Technology (KIHBT)*

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

HIGHER DIPLOMA IN ELECTRICAL POWER ENGINEERING

EEP 3304 : POWER SYSTEMS ENGINEERING III

SEMESTER EXAMINATIONS

SERIES: AUGUST/SEPTEMBER 2011

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer booklet*
- *Non-programmable calculator*

Answer Question **ONE (COMPULSORY)** in **section I** and any other **TWO** questions from **Section II**

This paper consists of **THREE** printed pages

SECTION I (compulsory – 30 marks)

Question 1

- a) (i) State conditions necessary for operating generators in parallel (4 marks)
- (ii) Explain the effect on generator output KW on varying
- (i) Prime mover speed
 - (ii) Power factor
 - (iii) Excitation (6 marks)
- b) Two 3phase 6.6kv star connected alternators supply a load of 3.0 MW at 0.8lag in a 1:2 ratio. The synchronous impedance per phase of machine X = $(0.8 + j30)$ ohms and that of Y = $(0.6 + j 14)$ ohms. The excitation of machine X is adjusted so that it delivers 200A at a lagging p.f.
- Determine for each machine
- (i) Current
 - (ii) P.f (12 marks)
- c) Briefly explain the following compensation methods of long overhead lines
- (i) Series
 - (ii) Shunt
 - (iii) Synchro
 - (iv) Transformer tap (8 marks)

SECTION II (Answer any TWO questions – 40 marks)

Question 2

- a) List any **THREE** factors that affect sag (3 marks)
- b) A conductor hangs in the form of a catenary $Y = C \cosh x/c$ where $c = 1525m$. The span is 305m and conductor weighs 1.49kg/m. Calculate:
- (i) Length of conductor
 - (ii) Sag
 - (iii) Maximum and minimum values of tension using the catenary method (17 marks)

Question 3

- a) Draw the equivalent circuit and the phasor diagrams for a nominal 'T' method of line representation (5 marks)
- b) A three phase 50HZ overheadline is 100km long. The phase values of resistance inductance and capacitance per km are 0.15ohm; 1.2mH; $0.008 \frac{\mu F}{\pi}$. The line supplies a load of 70MW; 0.8 lag at 132KV. Using the nominal π method, calculate:
- (i) Line efficiency

- (ii) Total line loss (15 marks)

Question 4

- a) State the main reason for 'short circuit fault level' studies (3 marks)
- b) For the system below, take 40MVA and 6.6 KV as base ratings and calculate for a 3phase balanced fault

- (i) Short circuit current and MVA fault level at F_1
(ii) Short circuit current and MVA fault level at F_2 (17 marks)

Question 5

- a) Compare arc extinction process for the following circuit breakers:
(i) Bulk oil; plain break
(ii) Bulk oil; explosion pot
(iii) SF₆ Gas blast (6 marks)
- b) With aid of a breaker oscillogram indicate the following
(i) Peak restriking voltage
(ii) Recovery voltage
(iii) Arc voltage
(iv) Current zero (10 marks)
- c) State:
(i) **TWO** methods used for voltage equalization across circuit breaker poles

(ii) The **TWO** major operational disadvantages of the SF6 circuit breaker (4 marks)